Bionic Circuit Diagram

AA Battery x 4

Servo Motor

Brown = GND (Ground)
Red = 5v (Power)
Orange = Pin 9 (Data)

Breadboard

Connections are
made across
these pins

Screw Terminal

Arduino